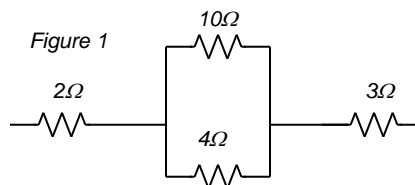


Physics

Unit 9: Electric Circuits

1. What is emf, kWh, rms, current, resistance, resistivity, and potential difference?
2. How do you use ammeters and voltmeters?
3. Know what factors your body's sensitivity to electricity?
4. Use Kirchhoff's Laws to solve problems.
5. A 2-A current flows through a circuit. How much charge passes a point during 1 minute?
6. A flashlight bulb is connected to a 3.0 V battery and a current of .020A flows. What is the resistance of the bulb's filament?
7. The resistivity of a metal is $3 \times 10^{-8} \Omega \cdot m$. The radius of the wire is 2 mm. If the length of the wire is 3 m, what is the resistance of the wire?
8. A 2-A current flows through a circuit with a resistance of 5Ω . How much energy is dissipated in 3 s?
9. A 2-A current flows through a circuit that consists of a resistor and an ideal battery. If the battery supplies 400 W, how large is the resistor?
10. An AC voltage has a rms value of 5.66. Determine the peak value of the voltage?
11. Three resistors, $2-\Omega$, $3-\Omega$, $4-\Omega$, are connected in series. What is the equivalent resistance of the series?
12. Two $10-\Omega$ and four $30-\Omega$ light bulbs are connected in series with a 9 V battery. What is the current that passes through each bulb?
13. Three resistors, $2-\Omega$, $3-\Omega$, $4-\Omega$, are connected in parallel. What is the equivalent resistance of the combination?
14. What is the equivalent resistance of figure 1



15. A non-ideal battery has a 12.0 V emf and internal resistance of 4Ω . Determine the terminal voltage of the battery when 2 A is drawn.
16. An uncharged 10 F capacitor and a resistor are connected in series to a 9 V battery and an open switch to form a simple RC circuit. The switch is closed at $t = 0$ s. The time constant of the circuit is 30 s. A) How big is the resistor and B) what is the maximum charge on the capacitor?

5. $I = \frac{q}{t}$
 $2A = \frac{q}{60s}$
 $q = \mathbf{120\ C}$
6. $V = IR$
 $3V = (0.02\ A)R$
 $R = \mathbf{150\ \Omega}$
7. $R = \rho \left(\frac{L}{A} \right)$
 $A = \pi r^2 = \pi(0.002\ m)^2 = 1.256 \times 10^{-5}\ m^2$
 $R = (3 \times 10^{-8}\ \Omega m) \left(\frac{3\ m}{1.256 \times 10^{-5}\ m^2} \right) = \mathbf{7.16 \times 10^{-3}\ \Omega}$
8. $P = I^2 R$
 $P = (2\ A)^2(5\ \Omega) = 20\ W$
 $P = \frac{W}{t}$
 $20\ W = \frac{W}{3s}$
 $W = \mathbf{60\ J}$
9. $P = I^2 R$
 $400\ W = (2\ A)^2 R$
 $R = \mathbf{100\ \Omega}$
10. $V_{rms} = \frac{V}{\sqrt{2}}$
 $5.66\ V = \frac{V}{\sqrt{2}}$
 $V = \mathbf{8.0\ V}$
11. $R_S = R_1 + R_2 + R_3$
 $R_S = 2\ \Omega + 3\ \Omega + 4\ \Omega = \mathbf{9\ \Omega}$
12. $R_S = R_1 + R_2 + R_3 + R_4 + R_5 + R_6$
 $R_S = 2 \cdot (10\ \Omega) + 4 \cdot (30\ \Omega) = 140\ \Omega$
 $V = IR$
 $9\ V = I(140\ \Omega)$
 $I = \mathbf{6.43 \times 10^{-2}\ A}$
13. $\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
 $\frac{1}{R_P} = \frac{1}{2\ \Omega} + \frac{1}{3\ \Omega} + \frac{1}{4\ \Omega}$
 $\frac{1}{R_P} = \frac{6}{12\ \Omega} + \frac{4}{12\ \Omega} + \frac{3}{12\ \Omega} = \frac{13}{12\ \Omega}$
 $R_P = \frac{\mathbf{12}}{\mathbf{13}}\ \Omega$
14. *Combine Parallel (middle)*
 $\frac{1}{R_P} = \frac{1}{10\ \Omega} + \frac{1}{4\ \Omega} = \frac{7}{20\ \Omega}$
 $R_P = \frac{\mathbf{20}}{\mathbf{7}}\ \Omega$
Combine Series
 $R_S = 2\ \Omega + \frac{20}{7}\ \Omega + 3\ \Omega = \frac{\mathbf{55}}{\mathbf{7}}\ \Omega$
15. *Internal*
 $V = IR = (2\ A)(4\ \Omega) = 8\ V$
Terminal
terminal = emf - internal
 $12\ V - 8\ V = \mathbf{4\ V}$
16. a. $\tau = RC$
 $30\ s = R(10\ F)$
 $R = \mathbf{3\ \Omega}$
 b. $Q = CV$
 $Q = (9\ V)(10\ F) = \mathbf{90\ C}$