

**Current**


- \_\_\_\_\_ of \_\_\_\_\_ of \_\_\_\_\_
- Amount of \_\_\_\_\_ per unit \_\_\_\_\_ that crosses one \_\_\_\_\_

$$I = \frac{\Delta Q}{\Delta t}$$

- Symbol: (\_\_\_\_\_)
- Unit: \_\_\_\_\_ (A)

Small computer speakers often have power supplies that give 12 VDC at 200 mA. How much charge flows through the circuit in 1 hour and how much energy is used to deliver this charge?

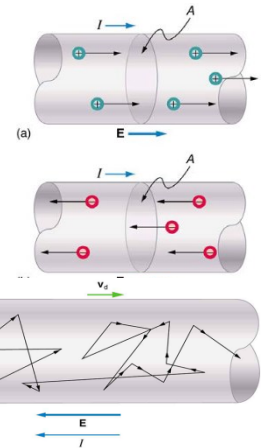- Electrons are the \_\_\_\_\_ that \_\_\_\_\_ through \_\_\_\_\_
- Historically thought \_\_\_\_\_ charges move
- \_\_\_\_\_ current is the \_\_\_\_\_ flow of \_\_\_\_\_ charges
- Flows from \_\_\_\_\_ terminal and into \_\_\_\_\_ terminal
- \_\_\_\_\_ current flows the \_\_\_\_\_ way



**Drift Velocity**

- \_\_\_\_\_ signals travel near \_\_\_\_\_ of \_\_\_\_\_, but \_\_\_\_\_ travel much \_\_\_\_\_
- Each new electron \_\_\_\_\_ one ahead of it, so current is actually like \_\_\_\_\_


$$I = \frac{\Delta Q}{\Delta t} = qnAv_d$$

- $q$  = charge of each electron,  $n$  = free charge density,  $A$  = cross-sectional area,  $v_d$  = drift velocity

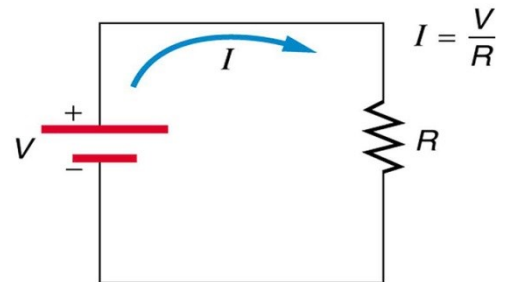**Ohm's Law**

$$I = \frac{V}{R} \text{ or } V = IR$$

- $V$  = emf,  $I$  = current,  $R$  = resistance
- Unit:  $V/A =$  \_\_\_\_\_ ( $\Omega$ )



**Resistors**


- Device that offers \_\_\_\_\_ to \_\_\_\_\_ of charges
- \_\_\_\_\_ wire has very \_\_\_\_\_ resistance
- Symbols used for \_\_\_\_\_



Our speakers use 200 mA of current at maximum volume. The voltage is 12V. The current is used to produce a magnet which is used to move the speaker cone. Find the resistance of the electromagnet.
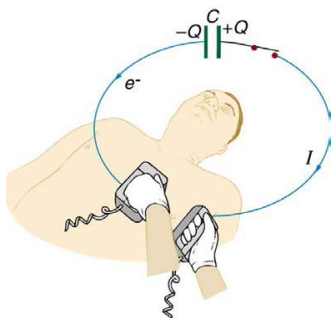
## Practice Work

- Can a wire carry a current and still be neutral—that is, have a total charge of zero? Explain.
- Car batteries are rated in ampere-hours (A·h). To what physical quantity do ampere-hours correspond (voltage, charge, ...), and what relationship do ampere-hours have to energy content?
- Why are two conducting paths from a voltage source to an electrical device needed to operate the device?
- In cars, one battery terminal is connected to the metal body. How does this allow a single wire to supply current to electrical devices rather than two wires?
- The IR drop across a resistor means that there is a change in potential or voltage across the resistor. Is there any change in current as it passes through a resistor? Explain.
- What is the current in milliamperes produced by the solar cells of a pocket calculator through which 4.00 C of charge passes in 4.00 h? (OpenStax 20.1) **0.278 mA**
- A total of 600 C of charge passes through a flashlight in 0.500 h. What is the average current? (OpenStax 20.2) **333 mA**
- What is the current when a typical static charge of 0.250  $\mu\text{C}$  moves from your finger to a metal doorknob in 1.00  $\mu\text{s}$ ? (OpenStax 20.3) **0.250 A**
- Find the current when 2.00 nC jumps between your comb and hair over a 0.500- $\mu\text{s}$  time interval. (OpenStax 20.4) **4.00 mA**
- A defibrillator sends a 6.00-A current through the chest of a patient by applying a 10,000-V potential as in the figure below. What is the resistance of the path? (OpenStax 20.7a) **1.67 k $\Omega$**
- During open-heart surgery, a defibrillator can be used to bring a patient out of cardiac arrest. The resistance of the path is 500  $\Omega$  and a 10.0-mA current is needed. What voltage should be applied? (OpenStax 20.8) **5.00 V**
- (a) A defibrillator passes 12.0 A of current through the torso of a person for 0.0100 s. How much charge moves? (b) How many electrons pass through the wires connected to the patient? (See figure.) (OpenStax 20.9) **0.120 C,  $7.50 \times 10^{17}$  electrons**



- A clock battery wears out after moving 10,000 C of charge through the clock at a rate of 0.500 mA. (a) How long did the clock run? (b) How many electrons per second flowed? (OpenStax 20.10)  **$2.00 \times 10^7$  s,  $3.13 \times 10^{15}$  electrons/s**
- What current flows through the bulb of a 3.00-V flashlight when its hot resistance is 3.60  $\Omega$ ? (OpenStax 20.18) **0.833 A**
- Calculate the effective resistance of a pocket calculator that has a 1.35-V battery and through which 0.200 mA flows. (OpenStax 20.19) **6.75 k $\Omega$**
- (a) Find the voltage drop in an extension cord having a 0.0600- $\Omega$  resistance and through which 5.00 A is flowing. (b) A cheaper cord utilizes thinner wire and has a resistance of 0.300  $\Omega$ . What is the voltage drop in it when 5.00 A flows? (c) Why is the voltage to whatever appliance is being used reduced by this amount? What is the effect on the appliance? (OpenStax 20.22) **0.300 V, 1.50 V**
- A power transmission line is hung from metal towers with glass insulators having a resistance of  $1.00 \times 10^9 \Omega$ . What current flows through the insulator if the voltage is 200 kV? (OpenStax 20.23) **0.200 mA**