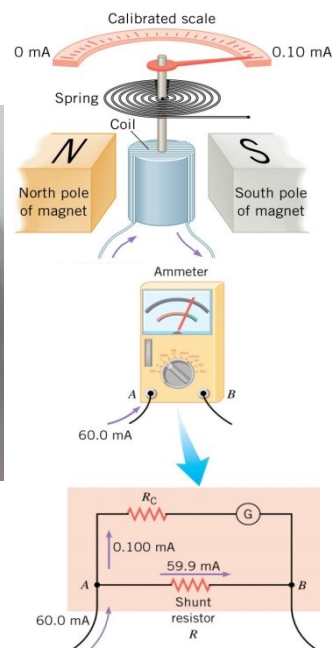


**DC Voltmeters and Ammeters**

- \_\_\_\_\_ (non-digital) meters
- Main component → \_\_\_\_\_


**Ammeters**

- Measures \_\_\_\_\_
- Inserted into \_\_\_\_\_ so \_\_\_\_\_ passes \_\_\_\_\_ it
- Connected in \_\_\_\_\_
- Coil usually measures only \_\_\_\_\_ current
- Has \_\_\_\_\_ connected in \_\_\_\_\_ to galvanometer so excess current can \_\_\_\_\_
- A \_\_\_\_\_ lets you \_\_\_\_\_ which shunt resistor is \_\_\_\_\_
- Problems with Ammeters
  - The \_\_\_\_\_ of the coil and shunt \_\_\_\_\_ add to the \_\_\_\_\_ of the circuit
  - This \_\_\_\_\_ the \_\_\_\_\_ in the circuit
  - \_\_\_\_\_ ammeter has \_\_\_\_\_ resistance
  - Real-life good \_\_\_\_\_ have \_\_\_\_\_ resistance so as only cause a \_\_\_\_\_ change in current



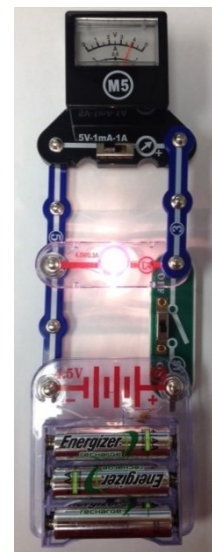**Voltmeters**

- Connected in \_\_\_\_\_ to \_\_\_\_\_ since parallel has same \_\_\_\_\_
- The coil works just like in the \_\_\_\_\_
- Given the \_\_\_\_\_ and the \_\_\_\_\_ of the coil → \_\_\_\_\_
- To give more range, a \_\_\_\_\_ resistor is connected in \_\_\_\_\_ with the coil
- Problems with Voltmeters
  - The voltmeter takes some the \_\_\_\_\_ out of the \_\_\_\_\_
  - \_\_\_\_\_ voltmeter would have \_\_\_\_\_ resistance as to draw \_\_\_\_\_ current
  - Good voltmeter has large \_\_\_\_\_ resistance as to make the \_\_\_\_\_ draw (and voltage drop) \_\_\_\_\_



**Practice Work**

- Suppose you are using a multimeter (one designed to measure a range of voltages, currents, and resistances) to measure current in a circuit and you inadvertently leave it in a voltmeter mode. What effect will the meter have on the circuit? What would happen if you were measuring voltage but accidentally put the meter in the ammeter mode?
- Specify the points to which you could connect a voltmeter to measure the following potential differences in Figure 1: (a) the potential difference of the voltage source; (b) the potential difference across  $R_1$ ; (c) across  $R_2$ ; (d) across  $R_3$ ; (e) across  $R_2$  and  $R_3$ . Note that there may be more than one answer to each part.
- To measure currents in Figure 1, you would replace a wire between two points with an ammeter. Specify the points between which you would place an ammeter to measure the following: (a) the total current; (b) the current flowing through  $R_1$ ; (c) through  $R_2$ ; (d) through  $R_3$ . Note that there may be more than one answer to each part.
- What is the sensitivity of the galvanometer (that is, what current gives a full-scale deflection) inside a voltmeter that has a  $1.00\text{-M}\Omega$  resistance on its  $30.0\text{-V}$  scale? (OpenStax 21.42)  **$30.0\ \mu\text{A}$**

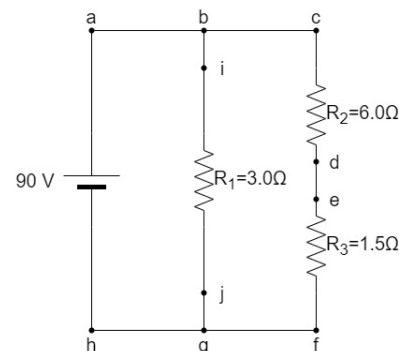


Figure 1

5. What is the sensitivity of the galvanometer (that is, what current gives a full-scale deflection) inside a voltmeter that has a  $25.0\text{-k}\ \Omega$  resistance on its 100-V scale? (OpenStax 21.43) **4.00 mA**
6. Find the resistance that must be placed in series with a  $25.0\text{-}\Omega$  galvanometer having a  $50.0\text{-}\mu\text{A}$  sensitivity to allow it to be used as a voltmeter with a 0.100-V full-scale reading. (OpenStax 21.44) **1.98 k $\Omega$**
7. Find the resistance that must be placed in series with a  $25.0\text{-}\Omega$  galvanometer having a  $50.0\text{-}\mu\text{A}$  sensitivity to allow it to be used as a voltmeter with a 3000-V full-scale reading. Include a circuit diagram with your solution. (OpenStax 21.45)  **$6.00 \times 10^7\ \Omega$**
8. Find the resistance that must be placed in parallel with a  $25.0\text{-}\Omega$  galvanometer having a  $50.0\text{-}\mu\text{A}$  sensitivity to allow it to be used as an ammeter with a 10.0-A full-scale reading. Include a circuit diagram with your solution. (OpenStax 21.46)  **$1.25 \times 10^{-4}\ \Omega$**
9. Find the resistance that must be placed in parallel with a  $25.0\text{-}\Omega$  galvanometer having a  $50.0\text{-}\mu\text{A}$  sensitivity to allow it to be used as an ammeter with a 300-mA full-scale reading. (OpenStax 21.47)  **$4.17 \times 10^{-3}\ \Omega$**