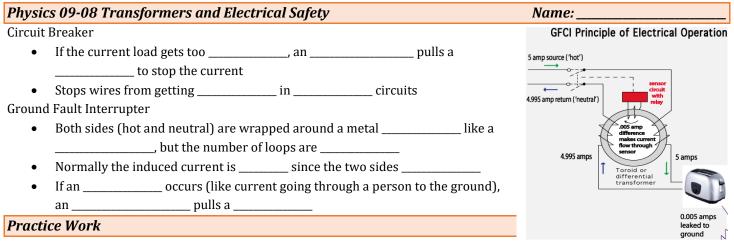


Created by Richard Wright – Andrews Academy

To be used with OpenStax High School Physics



- 1. Explain what causes physical vibrations in transformers at twice the frequency of the AC power involved.
- 2. Does plastic insulation on live/hot wires prevent shock hazards, thermal hazards, or both?
- 3. Why are ordinary circuit breakers and fuses ineffective in preventing shocks?
- A plug-in transformer supplies 9.00 V to a video game system. (a) How many turns are in its secondary coil, if its input voltage is 120 V and the primary coil has 400 turns? (b) What is its input current when its output is 1.30 A? (OpenStax 23.44) 30.0, 9.75 × 10<sup>-2</sup> A
- 5. An American traveler in New Zealand carries a transformer to convert New Zealand's standard 240 V to 120 V so that she can use some small appliances on her trip. (a) What is the ratio of turns in the primary and secondary coils of her transformer? (b) What is the ratio of input to output current? (c) How could a New Zealander traveling in the United States use this same transformer to power her 240 V appliances from 120 V? (OpenStax 23.45) **2.00, 0.500**
- 6. A cassette recorder uses a plug-in transformer to convert 120 V to 12.0 V, with a maximum current output of 200 mA. (a) What is the current input? (b) What is the power input? (c) Is this amount of power reasonable for a small appliance? (OpenStax 23.46) 20.0 mA, 2.40 W, yes
- 7. (a) What is the voltage output of a transformer used for rechargeable flashlight batteries, if its primary has 500 turns, its secondary 4 turns, and the input voltage is 120 V? (b) What input current is required to produce a 4.00 A output? (c) What is the power input? (OpenStax 23.47) **0.96 V, 32.0 mA, 3.84 W**
- 8. (a) The plug-in transformer for a laptop computer puts out 7.50 V and can supply a maximum current of 2.00 A. What is the maximum input current if the input voltage is 240 V? Assume 100% efficiency. (b) If the actual efficiency is less than 100%, would the input current need to be greater or smaller? Explain. (OpenStax 23.48) **0.063 A, greater**