
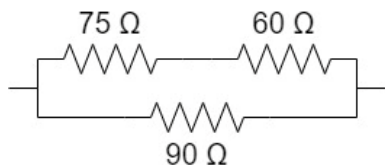


Physics Unit 8: Circuits Review

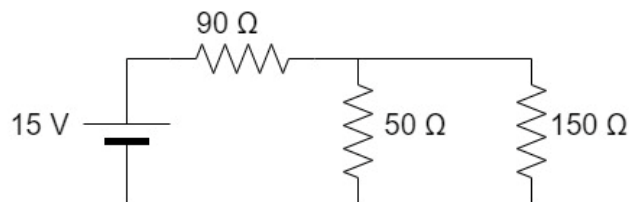1. Know about charge, current, potential, voltage, resistance, resistors, circuit diagrams, series, parallel, ammeters, voltmeters, power, kWh, AC/DC, thermal hazards, shock hazards
2. A 15-A current is maintained in a simple circuit with a total resistance of $2000\ \Omega$. What net charge passes through any point in the circuit during a 2-second interval?
3. When a light bulb is connected to a 24 V battery, a current of 0.2 A passes through the bulb filament. What is the resistance of the filament?
4. Three resistors, $100\text{-}\Omega$, $125\text{-}\Omega$, $150\text{-}\Omega$, are connected in series in a circuit. What is the equivalent resistance of this combination of resistors?
5. Ten $50\text{-}\Omega$ and five $25\text{-}\Omega$ light bulbs and a 9 V battery are connected in a series circuit. What is the current that passes through each bulb?
6. Three resistors, $100\text{-}\Omega$, $125\text{-}\Omega$, $150\text{-}\Omega$, are connected in parallel in a circuit. What is the equivalent resistance of this combination of resistors?
7. Two resistors, $50\text{-}\Omega$ and $25\text{-}\Omega$, are connected in parallel with a 24 V battery. What is the total current in the circuit?
8. Three resistors are connected as shown in the figure. The potential difference between points A and B is 12 V. What is the equivalent resistance between the points A and B?



Use the circuit diagram to answer 9 and 10.



9. What is the equivalent resistance of the circuit?
10. What is the current in the $90\ \Omega$ resistor?
11. A 15-A current is maintained in a simple circuit with a total resistance of $1500\ \Omega$. How much energy is dissipated in 5 seconds?
12. A 15-A current is maintained in a simple circuit that consists of a resistor between the terminals of an ideal battery. If the battery supplies energy at a rate of 75 W, how large is the resistance?
13. An AC current has a peak value of 8.49 A. Determine the rms value of the current.

Physics Unit 8: Circuits Review

Answers

2. $I = \frac{Q}{t}$
 $15 \text{ A} = \frac{Q}{2 \text{ s}}$
 $Q = \mathbf{30 \text{ C}}$
3. $V = IR$
 $24 \text{ V} = (0.2 \text{ A})R$
 $R = \mathbf{120 \Omega}$
4. $R_{eqv} = 100 \Omega + 125 \Omega + 150 \Omega = \mathbf{375 \Omega}$
5. Series has same current through all bulbs.
 $R_{eqv} = 10(50 \Omega) + 5(25 \Omega) = 625 \Omega$
 $V = IR_{eqv}$
 $9 \text{ V} = I(625 \Omega)$
 $I = \mathbf{0.0144 \text{ A}}$
6. $\frac{1}{R_{eqv}} = \frac{1}{100 \Omega} + \frac{1}{125 \Omega} + \frac{1}{150 \Omega}$
 $\frac{1}{R_{eqv}} = 0.02467 \frac{\square}{\Omega}$
 $R_{eqv} = \mathbf{40.5 \Omega}$
7. $\frac{1}{R_{eqv}} = \frac{1}{50 \Omega} + \frac{1}{25 \Omega}$
 $\frac{1}{R_{eqv}} = 0.06 \frac{\square}{\Omega}$
 $R_{eqv} = 16.7 \Omega$
 $V = IR_{eqv}$
 $24 \text{ V} = I(16.7 \Omega)$
 $I = \mathbf{1.44 \text{ A}}$
8. Do the series part first (most inside).
 $R_{series} = 75 \Omega + 60 \Omega$
 $R_{series} = 135 \Omega$
Combine the parallel branches.
 $\frac{1}{R_{eqv}} = \frac{1}{135 \Omega} + \frac{1}{90 \Omega}$
- $\frac{1}{R_{eqv}} = 0.0185 \frac{\square}{\Omega}$
 $R_{eqv} = \mathbf{54 \Omega}$
9. Combine the parallel branches.
 $\frac{1}{R_{parallel}} = \frac{1}{50 \Omega} + \frac{1}{150 \Omega}$
 $\frac{1}{R_{parallel}} = 0.0267 \frac{\square}{\Omega}$
 $R_{parallel} = 37.5 \Omega$
Combine that in series.
 $R_{eqv} = 90 \Omega + 37.5 \Omega$
 $R_{eqv} = \mathbf{127.5 \Omega}$
10. All the current from the battery goes through the 90 Ω resistor.
 $V = IR_{eqv}$
 $15 \text{ V} = I(127.5 \Omega)$
 $I = \mathbf{0.118 \text{ A}}$
11. $P = I^2 R$
 $P = (15 \text{ A})^2(1500 \Omega)$
 $P = 337500 \text{ W}$
 $P = \frac{W}{t}$
 $337500 \text{ W} = \frac{W}{5 \text{ s}}$
 $W = \mathbf{1.69 \times 10^6 \text{ J}}$
12. $P = I^2 R$
 $75 \text{ W} = (15 \text{ A})^2 R$
 $R = \mathbf{0.333 \Omega}$
13. $I_{rms} = \frac{I_0}{\sqrt{2}}$
 $I_{rms} = \frac{8.49 \text{ A}}{\sqrt{2}}$
 $I_{rms} = \mathbf{6.00 \text{ A}}$